

Design Procedure Using Sequential Circuit:

- Problem Description on State Diagram
- State Table
- State Reduction
- Assign Binary values to each state in state table
- Determine Number of flip-flops and assign a letter symbol to each
- Choose type of flip-flop to used
- From state table, derive Excitation table and Output table.

Design with Unused States:

A circuit with m -flip flops has 2^m states. When simplifying Input functions to flip-flops, the unused states can be treated as Don't Care Conditions.

State Reduction:

If 2 states have same input and output, they're equivalent states.

01 of the equivalent states can be reduced.

pdf [pg-224] Example

[pg-228] Example

↳ If goes to unused state, needs to be sent to used state

↳ Loop cannot be allowed to occur

Flip-Flop : S-R X

D-FlipFlop ✓

T-FlipFlop ✓

3-bit Gray Code Counter

① State Diagram

② State Table

Present State			Next State		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

③ Flip-Flop Transition Table/Excitation Table

Present State			Next State			D Flip-Flop		
C	B	A	C	B	A	E_c	E_B	E_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	1	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	1	0	1	1	0	1
1	0	1	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0

④ K-Maps

E_c

	$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
\bar{C}	0	0	0	1
C	0	1	1	1

Groupings: $\bar{B}\bar{A}$ (vertical), CA (horizontal)

$$E_c = \bar{B}\bar{A} + CA$$

E_B

	$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
\bar{C}	0	1	1	1
C	0	0	0	1

Groupings: $\bar{C}A$ (horizontal), $B\bar{A}$ (vertical)

$$E_B = \bar{C}A + B\bar{A}$$

E_A

	$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
\bar{C}	1	1	0	0
C	0	0	1	1

Groupings: $\bar{C}\bar{B}$ (horizontal), CB (vertical)

$$E_A = \bar{C}\bar{B} + CB$$

⑤ Logic Expressions for Inputs

⑥ Counter Implementation

Present State	Next State	A	B	C	D	E	F
0	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1
2	0	1	1	0	0	0	1
3	1	0	1	1	0	0	1
4	1	0	1	1	1	0	1
5	1	0	0	1	1	1	1
6	0	0	0	1	1	1	1
7	0	0	0	0	1	1	1


Present State	Next State	A	B	C	D	E	F
0	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1
2	0	1	1	0	0	0	1
3	1	0	1	1	0	0	1
4	1	0	1	1	1	0	1
5	1	0	0	1	1	1	1
6	0	0	0	1	1	1	1
7	0	0	0	0	1	1	1

$$E = BA + CA$$

$$F = CA + BA$$

$$A = CB + CA$$

State Diagram

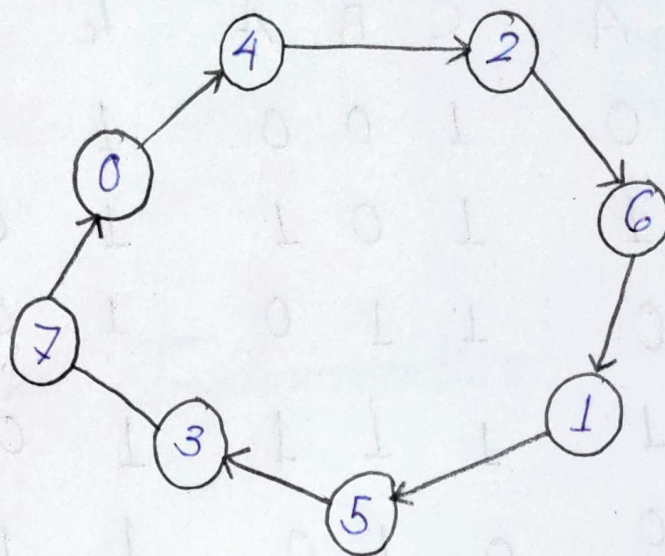

State Table:

	<u>Present State</u>				<u>Next State</u>		
	<u>C</u>	<u>B</u>	<u>A</u>		<u>C</u>	<u>B</u>	<u>A</u>
0	0	0	0	4	1	0	0
1	0	0	1	5	1	0	1
2	0	1	0	6	1	1	0
3	0	1	1	7	1	1	1
4	1	0	0	2	0	1	0
5	1	0	1	3	0	1	1
6	1	1	0	1	0	0	1
7	1	1	1	0	0	0	0

③ Flip Flop Transition Table / Excitation Table

Present State			Next State			T-Flip Flop		
C	B	A	C	B	A	T_C	T_B	T_A
0	0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0	0
0	1	0	1	1	0	1	0	0
0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0
1	0	1	0	1	1	1	1	0
1	1	0	0	0	1	1	1	1
1	1	1	0	0	0	1	1	1

④ K-Maps:

C \ BA				
	\bar{C}	C	\bar{C}	C
\bar{C}				
C				

$$T_C = 1$$

C \ BA				
	\bar{C}	C	\bar{C}	C
\bar{C}	0	0	0	0
C	1	1	1	1

$$T_B = C$$

C \ BA	$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
\bar{C}	0	0	0	0
C	0	0	1	1

$$T_A = CB$$

⑤ Logic Expressions for Inputs:

⑥ Counter Implementation:

